

# 苏州大学 VHDL 语言及应用期末答题卷(A 卷) 共 页

考试形式 开 卷 2020 年 06 月

院系 电子信息学院 年级 18 级 专业 通信工程

学号 1828401052 姓名 任彤 成绩

总 分	题 号	一	二	三	四	五	六	七
	题 分	60	20	20				
合分人	得 分							

得分

## 一. 课程教学目标 (共 60 分)

1.

(1) (9 分) 答案:

① 用 IF 改写:

```

ARCHITECTURE behav OF test1 IS
BEGIN
  PROCESS (s, a, b, c, d)
  BEGIN
    IF s = "00" THEN y <= a;
    ELSIF s = "01" THEN y <= b;
    ELSIF s = "10" THEN y <= c;
    ELSE y <= d;
  END IF;
  END PROCESS;
END behav;

```

② 用 when-else 改写:

```

ARCHITECTURE behav OF test1 IS
BEGIN
  y <= a when s = "00" ELSE
    b when s = "01" ELSE
    c when s = "10" ELSE
    d;
END behav;

```

③ 用 with-select 改写:

```

ARCHITECTURE behav OF test1 IS
BEGIN
  WITH s SELECT
    y <= a when "00",
    b when "01",
    c when "10",
    d;
END behav;

```

(2) (3 分) 答案:

(2) 组合电路。

该电路实现 4 选 1 多路选择器的功能, 不存在时序逻辑器件;  
且选择器是一个组合逻辑器件。

(3) (3 分) 答案:

(3) 该程序实现 4 选 1 多路选择器的功能, 当输入  $S = "00"$ , 输出  $a$ ; 输入  $"01"$ , 输出  $b$ ;  
输入  $"10"$ , 输出  $c$ , 其余输出  $d$ 。

2.

(1) (5 分) 答案:

2. (1) 内部组成: 门阵列,  $2^N$  个输入变量, 一路输出  
原理: 多路选择器。

(2) (5 分) 答案:

(2). (1)~(16) 内容:

0000 0000 00000011

3.

(1) (10 分) 答案:

```
3. (1) STD_LOGIC - ALL
    STD_LOGIC
    3 DOWNTO 0
    test2
    behav
    BEGIN
    clk
    q
    d
    END IF
```

(2) (3 分) 答案:

```
(2) ARCHITECTURE behav OF test2 IS
    SIGNAL a : STD_LOGIC_VECTOR(3 DOWNTO 0);
    BEGIN
    PROCESS (clk, load, d, input)
    BEGIN
    IF RISING_EDGE(clk) THEN
    IF (load = '1') THEN
    a <= input;
    else
    a(3) <= a(0);
    a(2) <= a(3);
    a(1) <= a(2);
    a(0) <= a(1);
    END IF;
    END IF;
    END PROCESS;
    q <= a;
    END behav;
```

(3) (2 分) 答案:

```
(3) LIBRARY IEEE;
    USE IEEE.STD_LOGIC_1164.ALL;
    ENTITY test2 IS
    PORT (clk, load, d : IN STD_LOGIC;
    input : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
    q : BUFFER STD_LOGIC_VECTOR(3 DOWNTO 0));
    END test2;
    ARCHITECTURE behav OF test2 IS
    BEGIN
    PROCESS (clk, load, d, input)
    BEGIN
    IF RISING_EDGE(clk) THEN
    IF (load = '1') THEN
    q <= input;
    else
    FOR i IN 2 DOWNTO 0 LOOP
    q(i) <= q(i+1);
    END LOOP;
    q(3) <= d;
    END IF;
    END PROCESS;
    END behav;
```

4.

(1) (10分) 答案:

4. (1)

```

1) 01  LIBRARY IEEE; (续加;)
2) 02  USE IEEE.STD_LOGIC_1164.ALL; (LOGIC和1164中间是-)
3) 05  Y: OUT STD_LOGIC_VECTOR (T DOWNTO 0); (TO改为DOWNTO)
4) 08  SIGNAL indata: STD_LOGIC_VECTOR (2 DOWNTO 0); (进程外,这里定义信号 SIGNAL)
5) 10  indata <= d2 & d1 & d0; (信号赋值 <=)
6) 11  PROCESS (indata, en) (Y是输出,不应在敏感信号表中).
7) 13  IF (en = '1') THEN (en是逻辑位,需加引号).
8) 24  END CASE; (CASE语句结尾为END CASE)
9) 26  Y <= "11111111"; (8位逻辑量用双引号)
10) 29 END rtl; (结构体名 rtl).


```

(2) (5分) 答案:

(2) 该程序实现3线-8线译码的功能。

输入3位二进制和一个使能信号,当使能信号为高电平,电路工作。根据3位二进制转换十进制的值,在对应的输出端口输出低电平,其它位为高电平。当使能信号不为高电平,电路不工作,输出8位全为高电平。

(3) (5分) 答案:

 

得分

## 二. 课程教学目标 (共 20 分)

1. (10 分) 答案:

```

二. 1. LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
ENTITY count12 IS
    PORT (clk, clr, en: IN STD_LOGIC;
          Q: OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
END count12;
ARCHITECTURE rtl OF count12 IS
    SIGNAL CQ: STD_LOGIC_VECTOR(3 DOWNTO 0);
    BEGIN
        PROCESS (clk, clr, en)
            BEGIN
                IF (clr='1') THEN
                    CQ <= "0000";
                ELSIF (clk'EVENT AND clk='1') THEN
                    IF (en='1') THEN
                        IF (CQ = "1011") THEN
                            CQ <= "0000";
                        ELSE
                            CQ <= CQ+1;
                        END IF;
                    END IF;
                END IF;
            END PROCESS;
            Q <= CQ;
        END rtl;

```

2. (10 分) 答案:

```

2. LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL; USE IEEE.STD_LOGIC_UNSIGNED.ALL;
ENTITY clkGEN IS
    PORT ( clk: IN STD_LOGIC;
          clk2div, clk4div: OUT STD_LOGIC);
END clkGEN;
ARCHITECTURE behav OF clkGEN IS
    SIGNAL div2, div4: STD_LOGIC;
    SIGNAL count: STD_LOGIC_VECTOR(1 DOWNTO 0);
    BEGIN
        PROCESS (clk)
            IF (clk'EVENT AND clk='1') THEN
                div2 <= not div2;
                IF (count="01") THEN
                    count <= (OTHERS => '0');
                    div4 <= not div4;
                ELSE
                    count <= count + 1;
                END IF;
            END IF;
        END PROCESS;
        clk2div <= div2;
        clk4div <= div4;
    END behav;

```

注: 若clk处输入 100MHz 时钟信号, clk2div 输出 50MHz, clk4div 输出 25MHz.

得分

三. 课程教学目标 (共 20 分)

1.

(1) (10 分) 答案:

三. 1. (1)

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
ENTITY monostable IS
    PORT (clk4, din, rst : IN STD_LOGIC;
          dout : OUT STD_LOGIC);
END monostable;

ARCHITECTURE behave OF monostable IS
    SIGNAL i : INTEGER;
    PROCESS (clk4, din, rst)
    BEGIN
        IF rst = '1' THEN dout <= '0';
        ELSIF (clk4'EVENT AND clk = '1') THEN
            IF (din = '1') THEN
                i <= 0;
                WHILE (i < 4) LOOP
                    IF (clk4'EVENT AND clk = '1') THEN
                        dout <= '1';
                        i <= i + 1;
                    END IF;
                END LOOP;
            END IF;
        END IF;
    END PROCESS;
END behave;
```

(2) (10 分) 答案:

```
(2) LIBRARY IEEE;
USE IEEE.STD-LOGIC-1164.ALL;

ENTITY PLL1 IS
    PORT ( clk4, pd_bef, pd_aft, rst: IN STD-LOGIC;
          clk_d2, clk_d1: IN STD-LOGIC;
          clk_in: OUT STD-LOGIC);
END PLL1;

ARCHITECTURE behav OF PLL1 IS
    COMPONENT monostable
        PORT (clk4, din, rst: IN STD-LOGIC;
              dout: OUT STD-LOGIC);
    END COMPONENT;
    SIGNAL a, b, c, d: STD-LOGIC;
    BEGIN
        u1: monostable PORT MAP (clk4, pd_bef, rst, a);
        u2: monostable PORT MAP (clk4, pd_aft, rst, b);
        c <= (NOT a) AND clk_d1;
        d <= b AND clk_d2;
        clk_in <= c OR d;
    END behav;
```